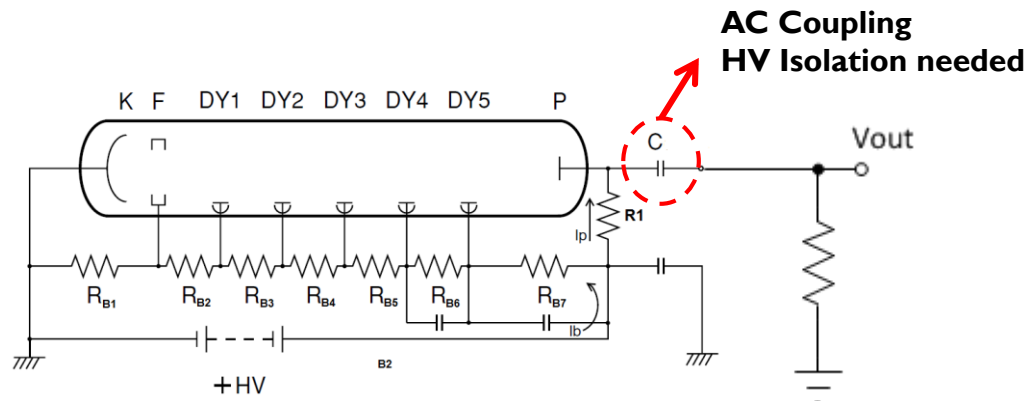


# **ENERGY PLANE FRONT END ELECTRONICS**


Canfranc May - 2016

# PMT – Connection Mode


## ► Grounded Cathode



## Conceptual Equivalent Circuit

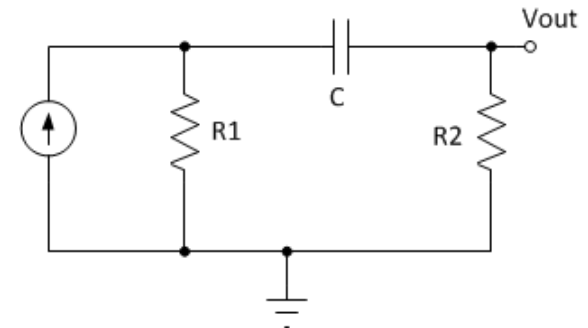

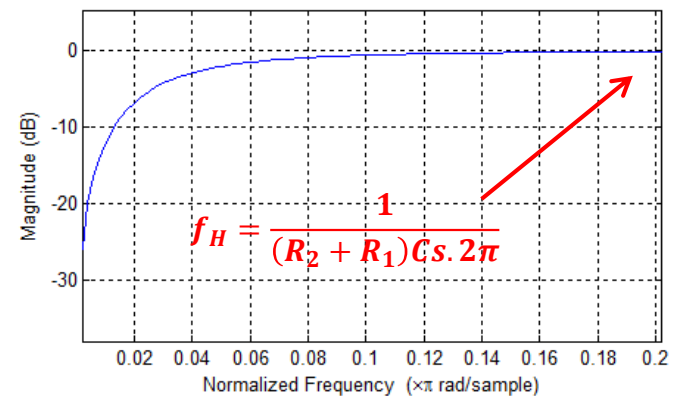
$$\frac{V_{out}}{I_i} = \left(R_2/R_1\right) \frac{(R_2 + R_1)Cs}{(R_2 + R_1)Cs + 1}$$



\* Hamamatsu PMT Handbook


# Coupling Capacitor Side Effects
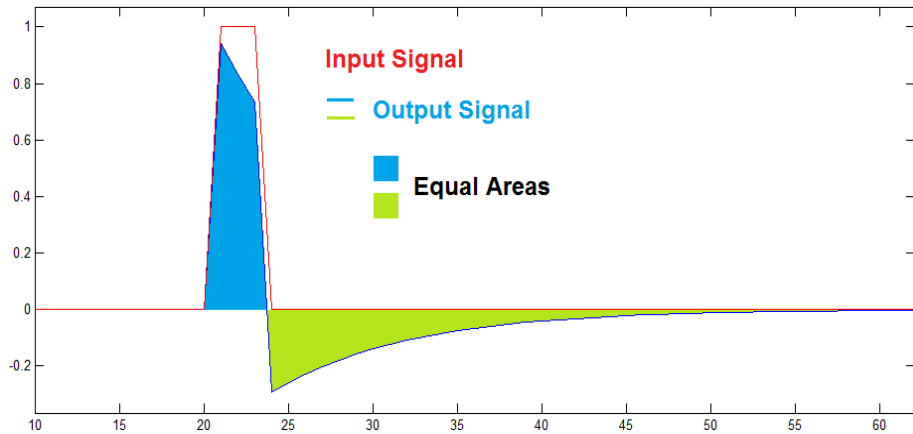
## ► Baseline Shift – Energy Resolution Effect in long signals (I)



Energy resolution for a Single Pulse is fine (although pulse length is longer)

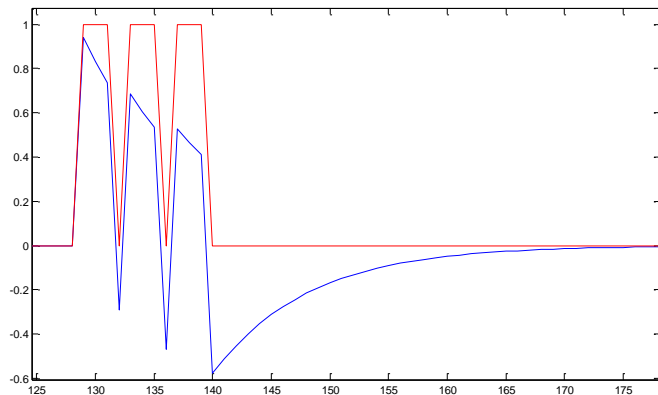
However, energy measurement based on area in long multipulse signals gets distorted by baseline shift.




**Example:** Total area including positive and negative lobes predicts 2.28 energy pulses

# Coupling Capacitor Side Effects
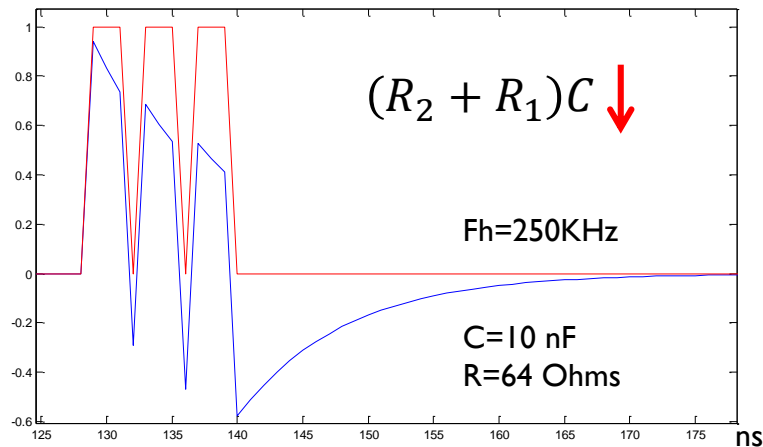
## ► Baseline Shift – Energy Resolution Effect in long signals (II)



~24% Energy Res

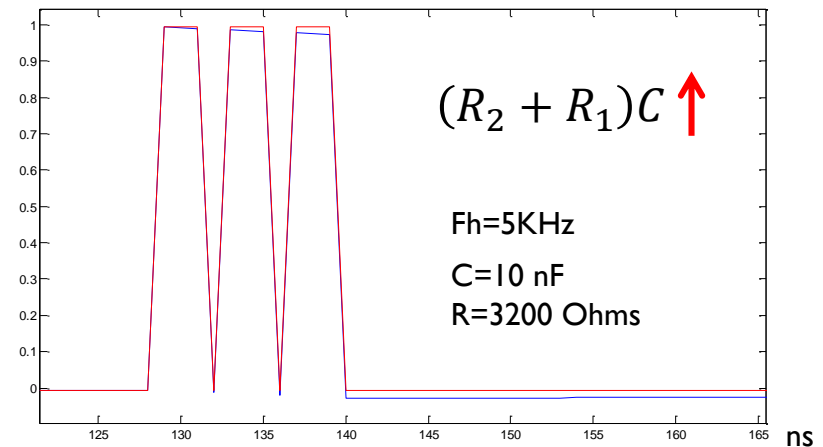


~2% Energy Res

Longer time constants relieve the loss in resolution  
However **high value HV Capacitors** are **difficult to find** and  
**big Resistors** introduce **thermal noise** issues

# Front End Concept

- ▶ Based on David Nygren's proposal.

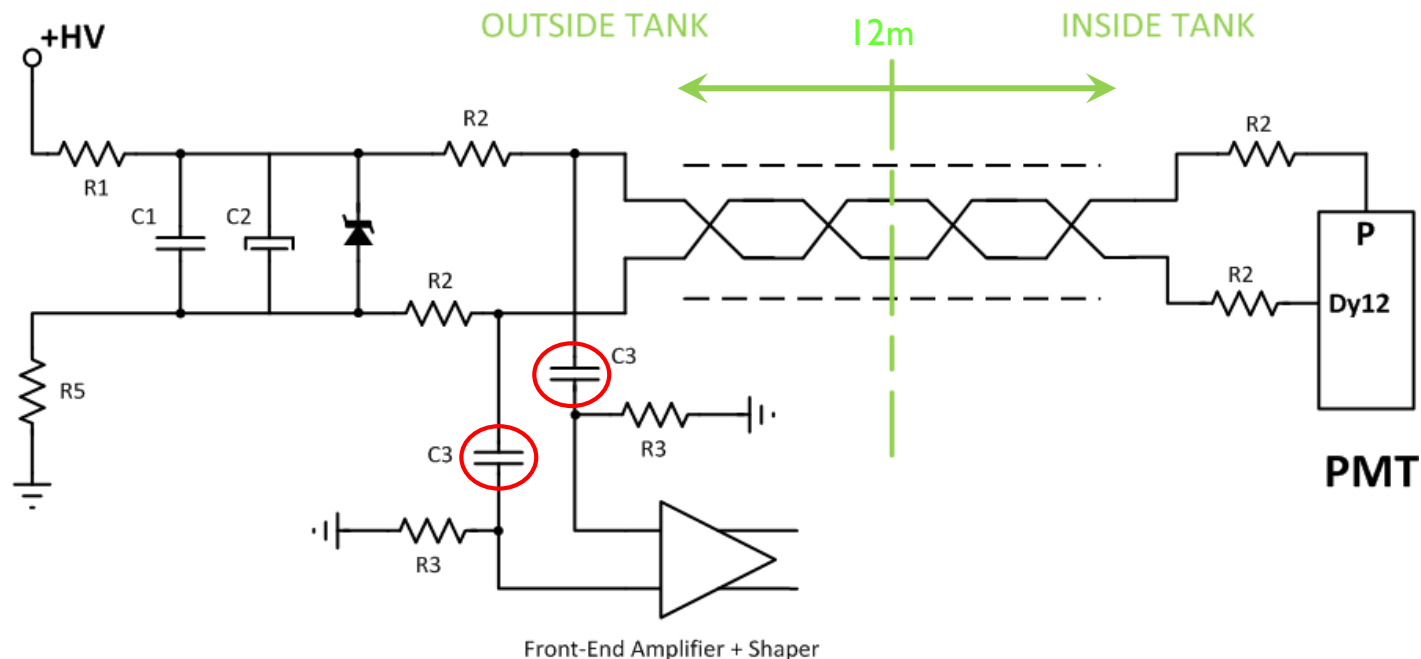

- ✓ P – Dy12 connection generates a pseudo-differential signal (increases induced noise immunity)
- ✓ R2 differential impedance matching (PMT ringing)
- ✓ Signal is generated by  $i(P)$  &  $i(Dy12)$  in R2
- ✓  $R3 * C3$  - A high HPF time constant will keep C3 from discharging thus reducing Baseline Shift

# The “Oscilloscope” Solution

## ► Coupling Capacitor Side Effects. Design Trade-Offs

### ► PMT – Single Photo Electron response

\* Due to FE  
Filtering Effect

\*Z<sub>in</sub> = 124  
(1/2 Match Loss)

PM_GAIN	4,50E+06
SPE_length	5,5 ns
SPE_lmax*	26 uA
SPE_charge	0,7 pC
SPE_in_V*	1,61 mV

### ► DAQ Facts

BANDWIDTH	10 MHz
ADC Dynamic Range	2 V
ADC_bits	12
ADC_LSB	0,49 mV
ADC_Gain	1,25
SPE_ADC	7,35 mV
SPE_LSB	15



## FRONT END BASIC SPECS

SPE_LSB	15
SPE_FE_out	5,88 mV
LSB_FE_out	0,392 mV
GAIN	226,5 Vout / lin


Noise(rms) should be  
kept under 1/2 LSB

Including R2 (A<sub>v</sub> ≈ 4)

# The “Oscilloscope” Solution

## ► Coupling Capacitor Side Effects. Design Trade-Offs

### Conceptual Equivalent Circuit

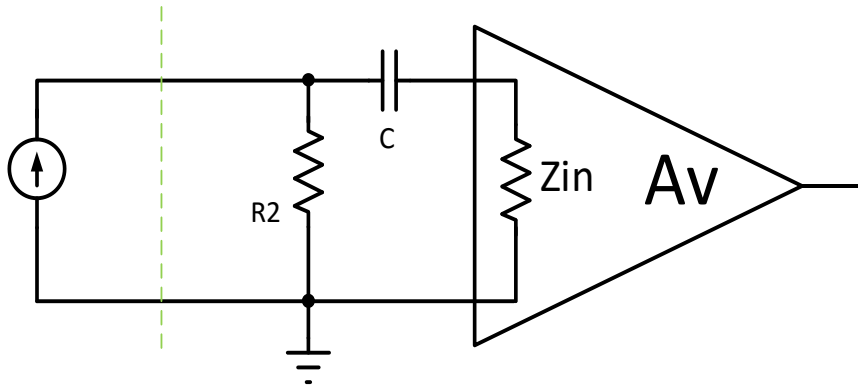


Pseudo Diff. introduces a remarkable Common Mode to be matched at the Amplifier.

SRF of Coupling capacitor should be higher than the expected Bandwidth of the FE  
→ Polypropylene / Ceramic CGO up to 10 nF are commercially available

# The “Oscilloscope” Solution
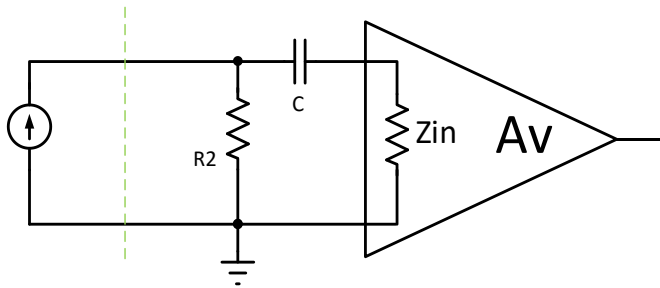
## ► Coupling Capacitor Side Effects. Design Trade-Offs




The **higher** the value of  **$Z_{in}$**  the **lower** the **baseline shift effect** in Energy measurement.

However **high values of  $Z_{in}$**  will increase **thermal noise** of the FE

A **generic FE model** has been developed which includes coupling, C shaping, DAQ quantization, finite precision effects and noise.

Simulations show that a  **$f_{min}$  lower than 10 Hz** is needed for a **Energy Resolution better than 1%**

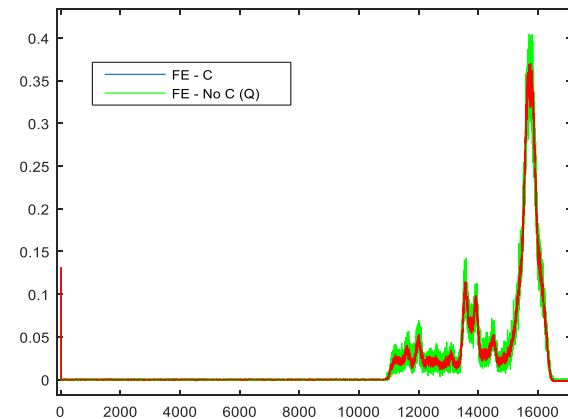→  $C = 10 \text{ nF}$  //  **$Z_{in} = 1.6 \text{ M}$**




**Thermal Noise (FE OUT) > 2 mVrms  $\approx$  5 LSB**

(only the  $Z_{in}$  noise considered)


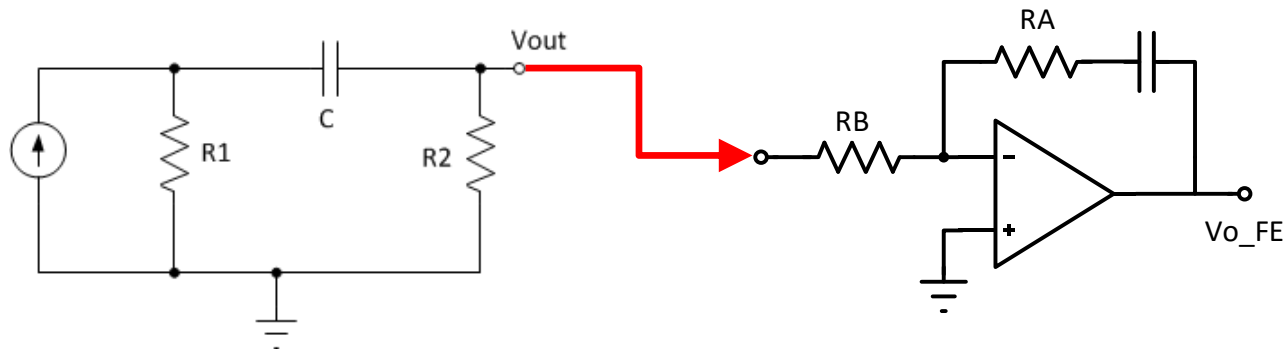
# Analog BLR Solution

- **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**



$$\frac{V_{out}}{I_i} = \left(R_2/R_1\right) \frac{(R_2 + R_1)Cs}{(R_2 + R_1)Cs + 1}$$


$$\frac{V_{out\_FE}}{V_{out}} = \frac{(R_A)Cs + 1}{(R_B)Cs} = \frac{R_A}{R_B} + \frac{1}{R_B Cs}$$

$$X(t) * H(t) = Y(t) \quad \longrightarrow \quad Y(t) * H^{-1}(t) = X(t)$$

$R_A$  and  $R_B$  can be designed so that the effect of the Coupling  $C$  is nullified
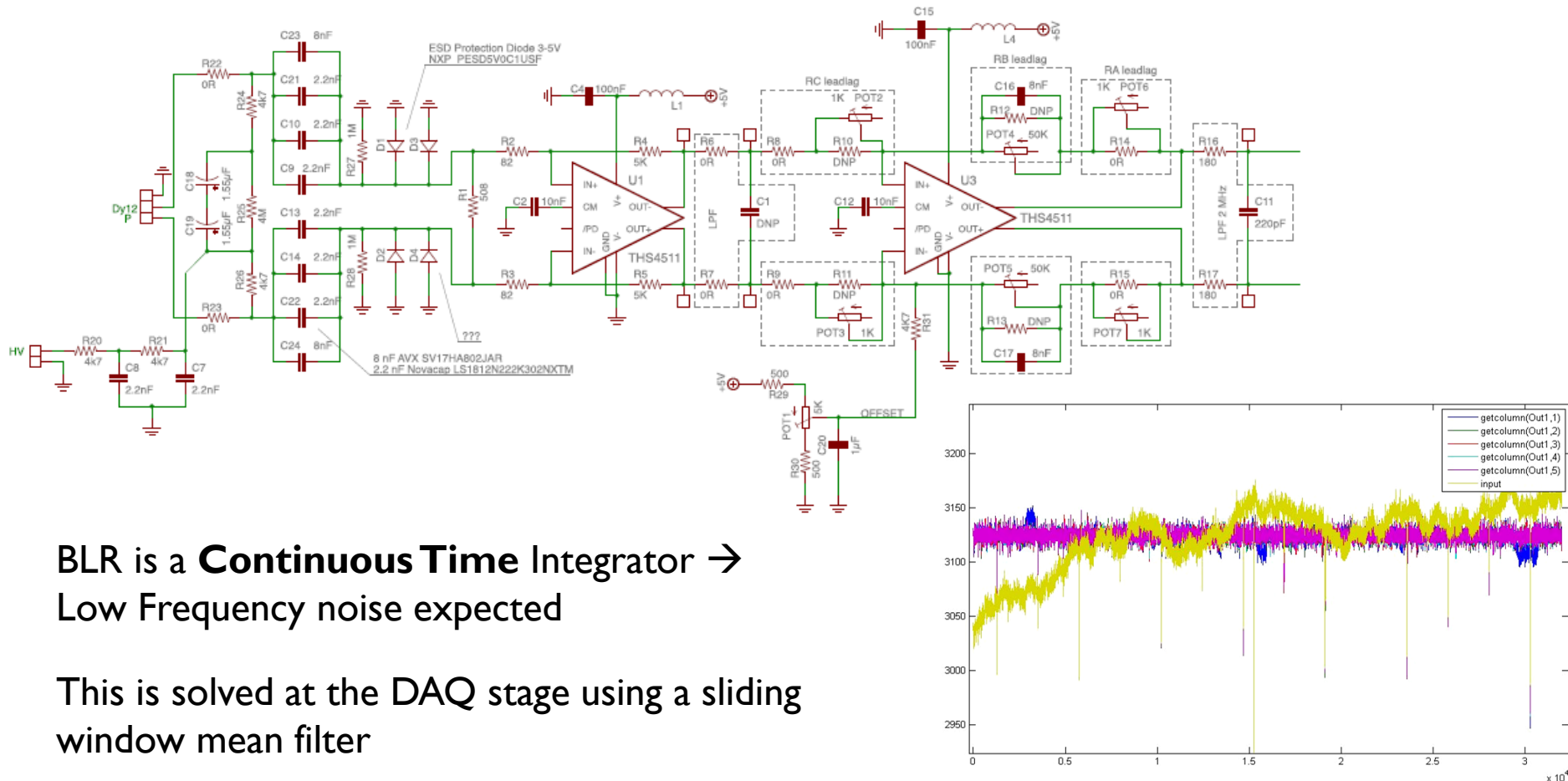
# Analog BLR Solution


- **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**



BLR is a **Continuous Time** Integrator →  
Low Frequency noise expected


This is solved at the DAQ stage using a sliding window mean filter

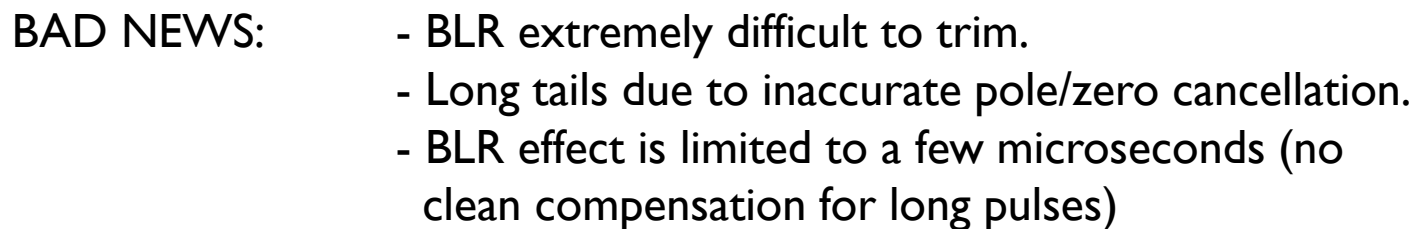► **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**





# Two Sides Solution

## ► Moderate RC + Digital BLR

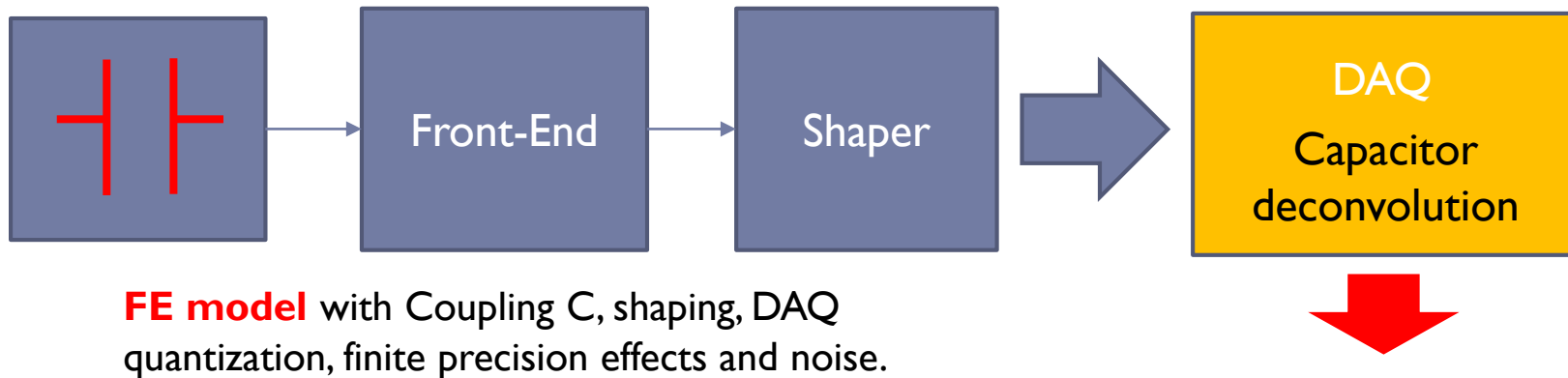

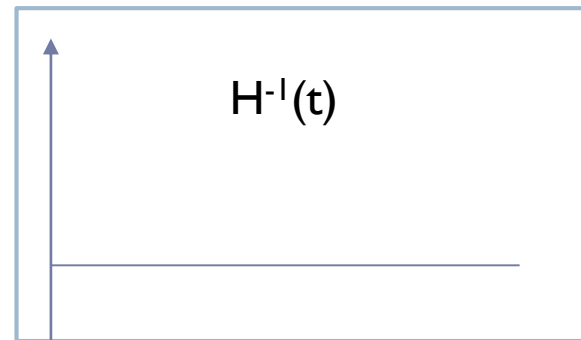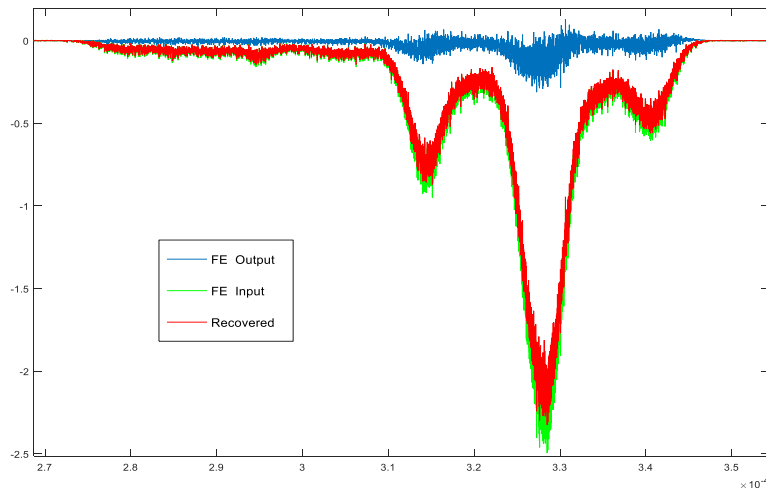**FE model** with Coupling C, shaping, DAQ quantization, finite precision effects and noise.




# Two Sides Solution

---

## ► Moderate RC + Digital BLR
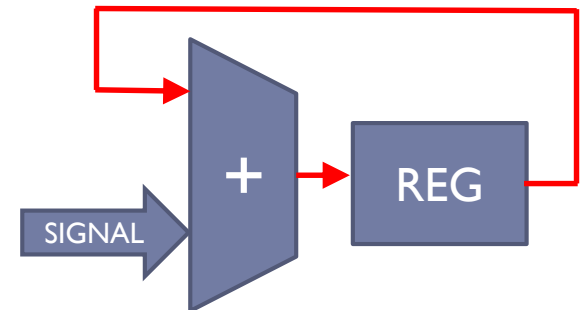
### ► IMPROVEMENTS:

- $Z_{in} \cdot C$  time constant ( $f_{HPB}$ ) can be relaxed → **Lower  $Z_{in}$  → Lower NOISE**
- Digital BLR can be switched off when no signal is detected and switched on when pulses are detected using a threshold → **No LF noise**
- Digital BLR implementation is very simple.  
NO NEED to use a FIR (MAC unit).



# Two Sides Solution



## ► PRELIMINARY RESULTS (Simulated)

- The Zin can be downsized to 2100 Ohms with this results:

**Thermal Noise\* (FE OUT) < 0.17 mVrms  $\approx$  0.43 LSB**  
**Estimated Energy Measurement Error < 0.64 %**

\* Fully-Diff Opamp Config. All noise sources considered

**SPECS  
FULFILLED !!!**

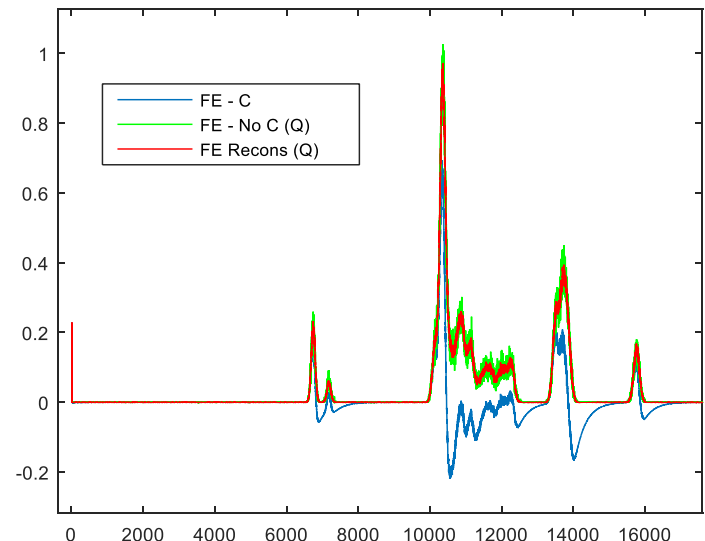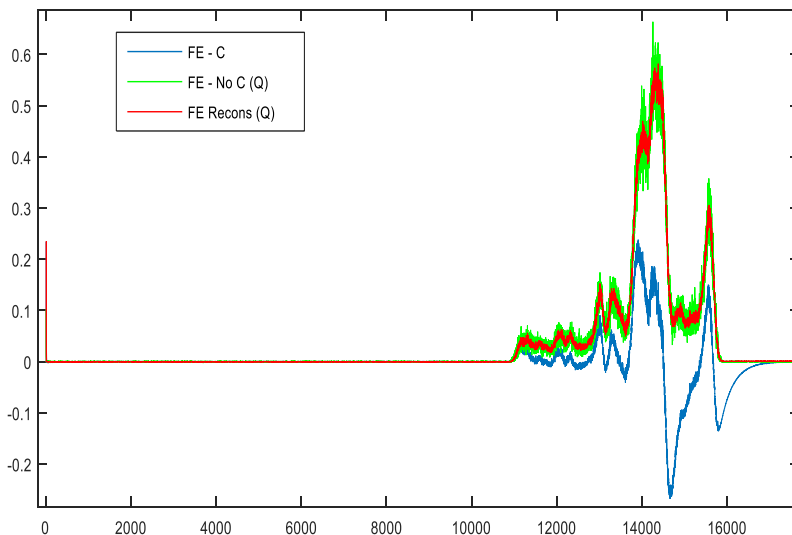

# Further Improvement

## ► Anode Preamp + Fully Differential Mode Transmission

