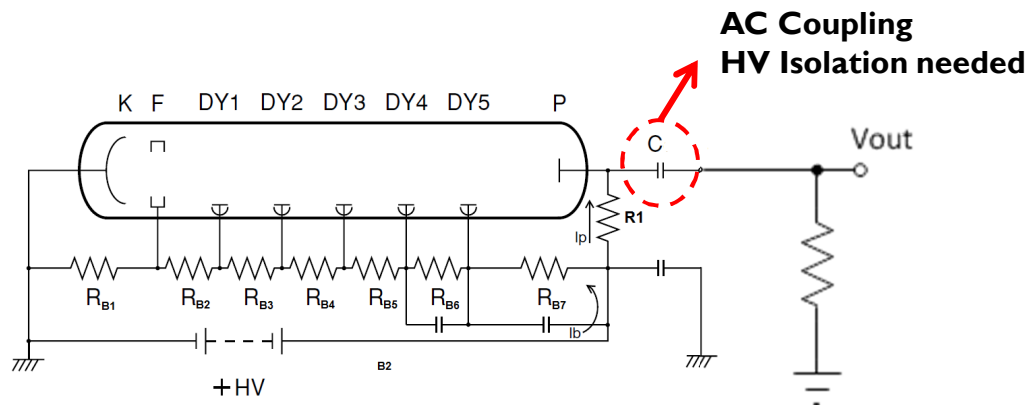


ENERGY PLANE FRONT END ELECTRONICS


Canfranc May - 2016

PMT – Connection Mode


► Grounded Cathode



Conceptual Equivalent Circuit

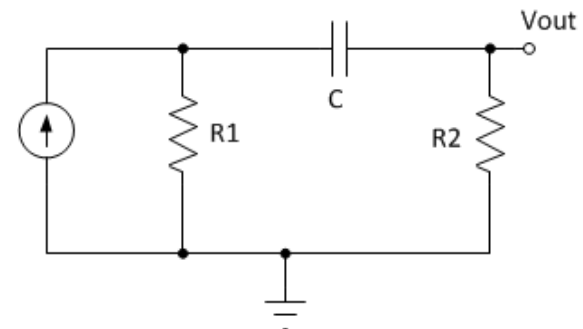

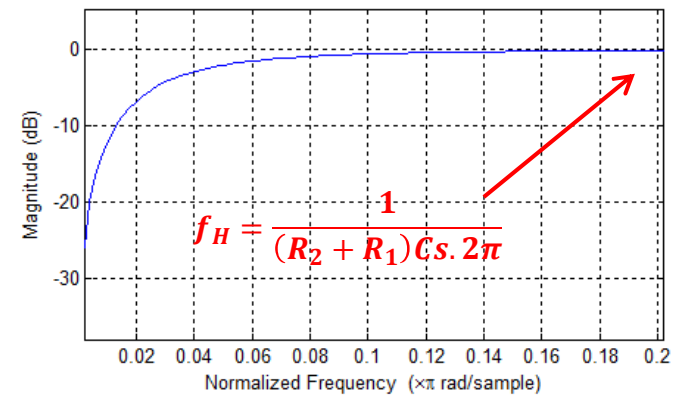
$$\frac{V_{out}}{I_i} = \left(R_2/R_1\right) \frac{(R_2 + R_1)Cs}{(R_2 + R_1)Cs + 1}$$



* Hamamatsu PMT Handbook


Coupling Capacitor Side Effects

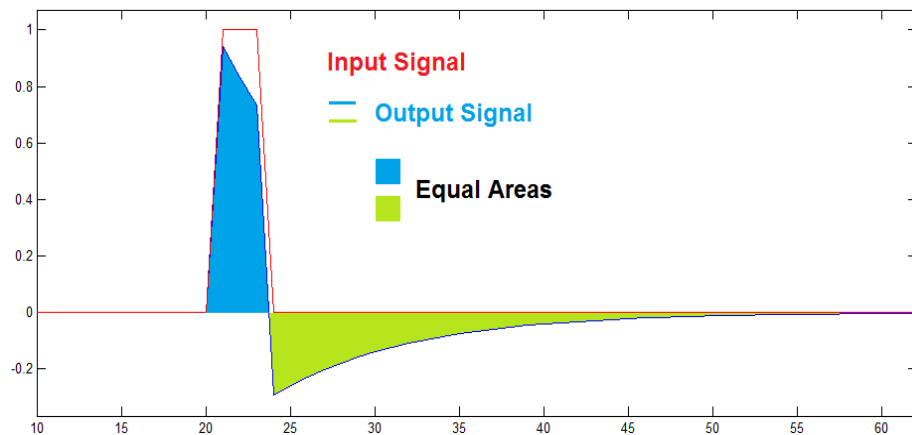► Baseline Shift – Energy Resolution Effect in long signals (I)



Energy resolution for a Single Pulse is fine (although pulse length is longer)


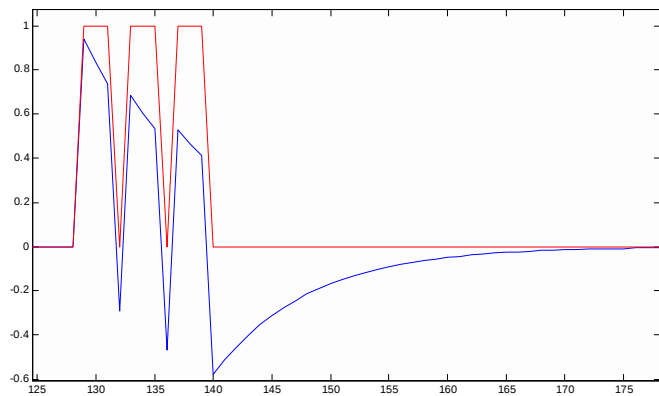
However, energy measurement based on area in long multipulse signals gets distorted by baseline shift.



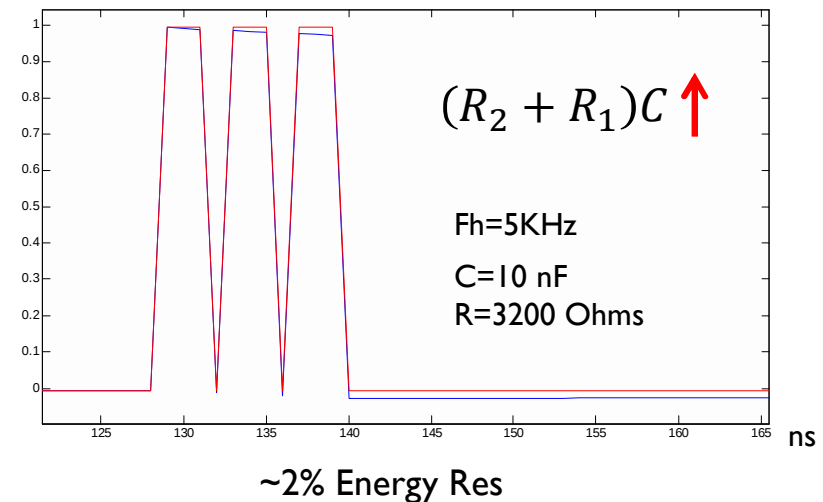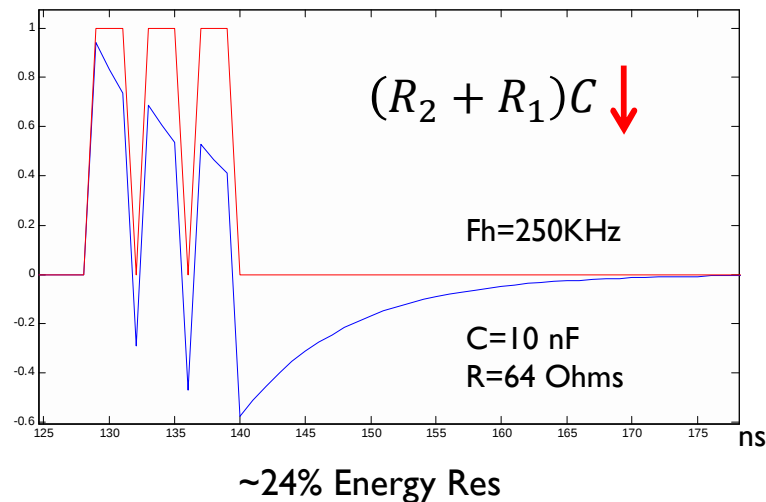Example: Total area including positive and negative lobes predicts 2.28 energy pulses

Coupling Capacitor Side Effects


► Baseline Shift – Energy Resolution Effect in long signals (II)



Longer time constants relieve the loss in resolution
However **high value HV Capacitors** are **difficult to find** and
big Resistors introduce **thermal noise** issues

Front End Concept

- ▶ Based on David Nygren's proposal.

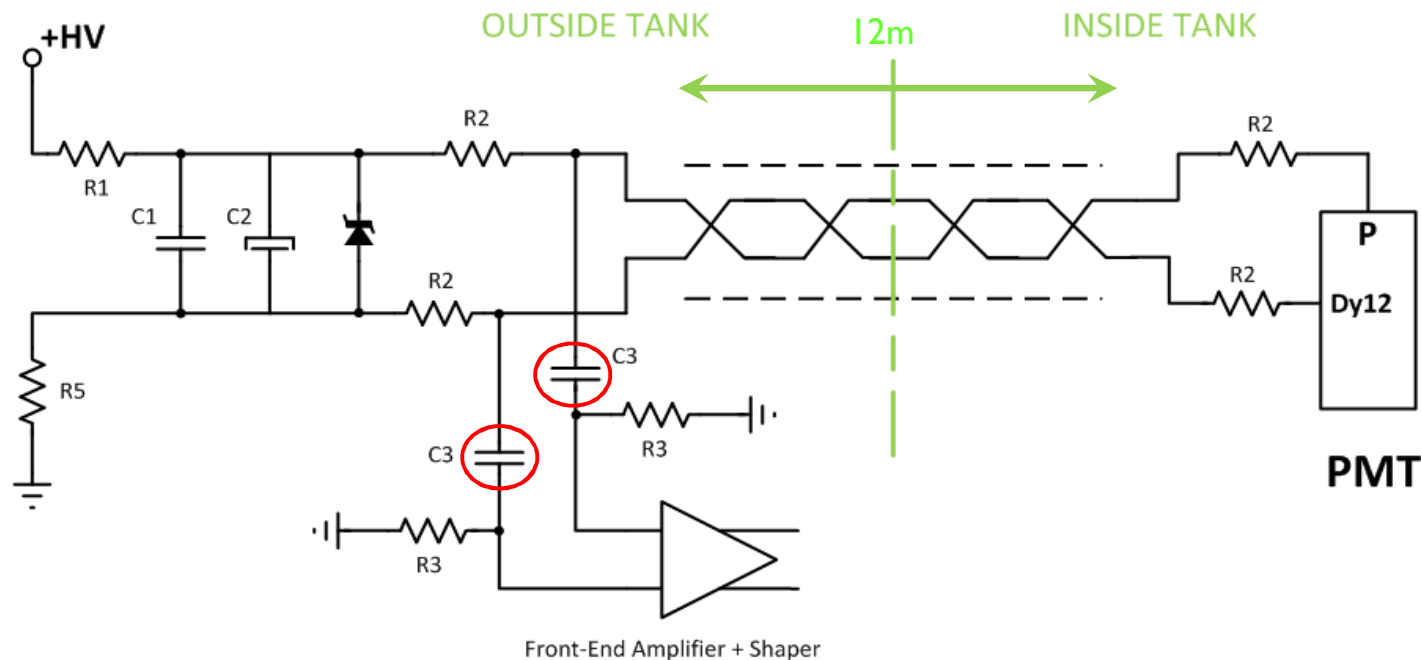

- ✓ P – Dy12 connection generates a pseudo-differential signal (increases induced noise immunity)
- ✓ R2 differential impedance matching (PMT ringing)
- ✓ Signal is generated by $i(P)$ & $i(Dy12)$ in R2
- ✓ $R3 * C3$ - A high HPF time constant will keep C3 from discharging thus reducing Baseline Shift

The “Oscilloscope” Solution

► Coupling Capacitor Side Effects. Design Trade-Offs

► PMT – Single Photo Electron response

* Due to FE
Filtering Effect

*Z_{in} = 124
(1/2 Match Loss)

PM_GAIN	4,50E+06
SPE_length	5,5 ns
SPE_lmax*	26 uA
SPE_charge	0,7 pC
SPE_in_V*	1,61 mV

► DAQ Facts

BANDWIDTH	10 MHz
ADC Dynamic Range	2 V
ADC_bits	12
ADC_LSB	0,49 mV
ADC_Gain	1,25
SPE_ADC	7,35 mV
SPE_LSB	15



FRONT END BASIC SPECS

SPE_LSB	15
SPE_FE_out	5,88 mV
LSB_FE_out	0,392 mV
GAIN	226,5 Vout / lin


Noise(rms) should be
kept under 1/2 LSB

Including R2 (A_v ≈ 4)

The “Oscilloscope” Solution

- ▶ Coupling Capacitor Side Effects. Design Trade-Offs

Conceptual Equivalent Circuit

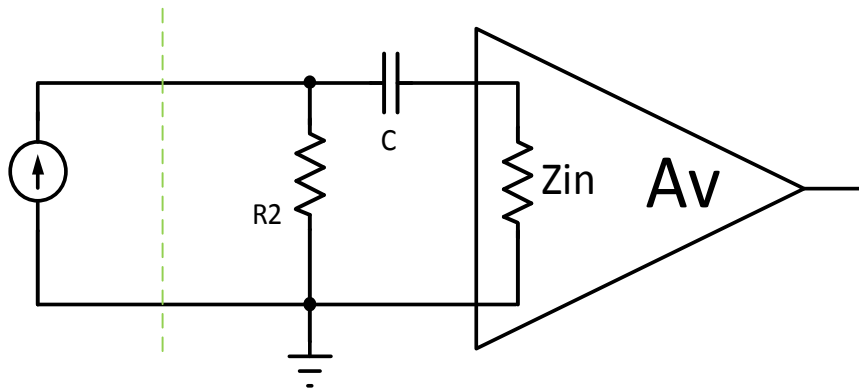


Pseudo Diff. introduces a remarkable Common Mode to be matched at the Amplifier.

SRF of Coupling capacitor should be higher than the expected Bandwidth of the FE
→ Polypropylene / Ceramic CGO up to 10 nF are commercially available

The “Oscilloscope” Solution

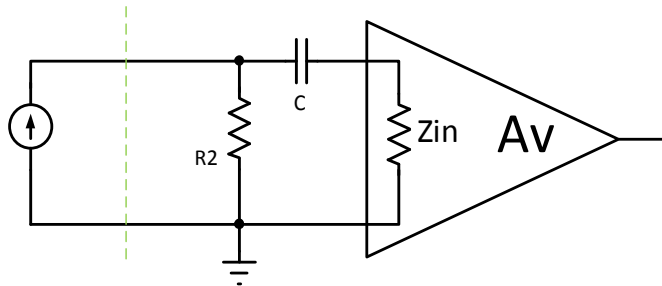► Coupling Capacitor Side Effects. Design Trade-Offs




The **higher** the value of **Zin** the **lower** the **baseline shift** effect in Energy measurement.

However **high values of Zin** will increase **thermal noise** of the FE

A **generic FE model** has been developed which includes coupling, C shaping, DAQ quantization, finite precision effects and noise.

Simulations show that a **f_{hmin} lower than 10 Hz** is needed for a **Energy Resolution better than 1%**

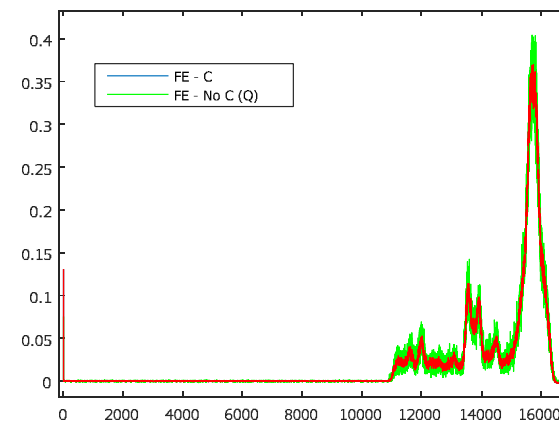→ $C = 10 \text{ nF}$ // $Z_{in} = 1.6 \text{ M}$




Thermal Noise (FE OUT) > 2 mVrms ≈ 5 LSB

(only the Zin noise considered)

Analog BLR Solution

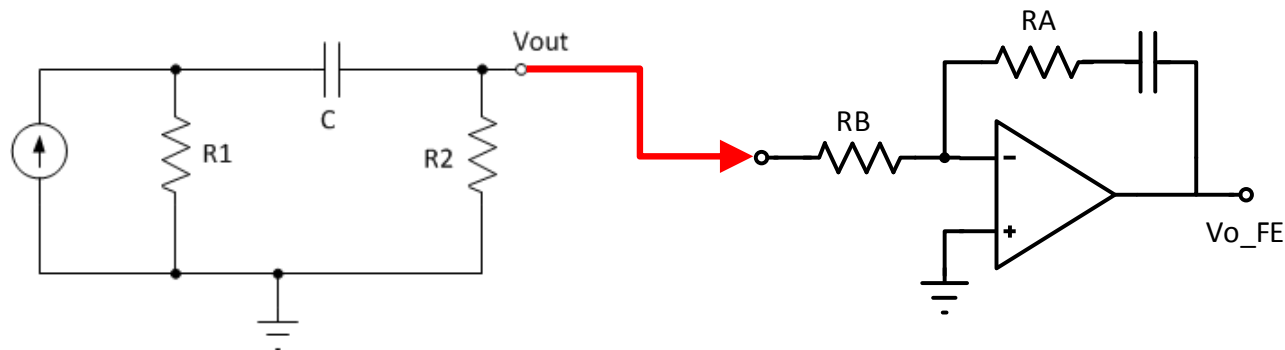- **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**



$$\frac{V_{out}}{I_i} = \left(R_2/R_1\right) \frac{(R_2 + R_1)Cs}{(R_2 + R_1)Cs + 1}$$


$$\frac{V_{out_FE}}{V_{out}} = \frac{(R_A)Cs + 1}{(R_B)Cs} = \frac{R_A}{R_B} + \frac{1}{R_B Cs}$$

$$X(t) * H(t) = Y(t) \quad \longrightarrow \quad Y(t) * H^{-1}(t) = X(t)$$

R_A and R_B can be designed so that the effect of the Coupling C is nullified

Analog BLR Solution

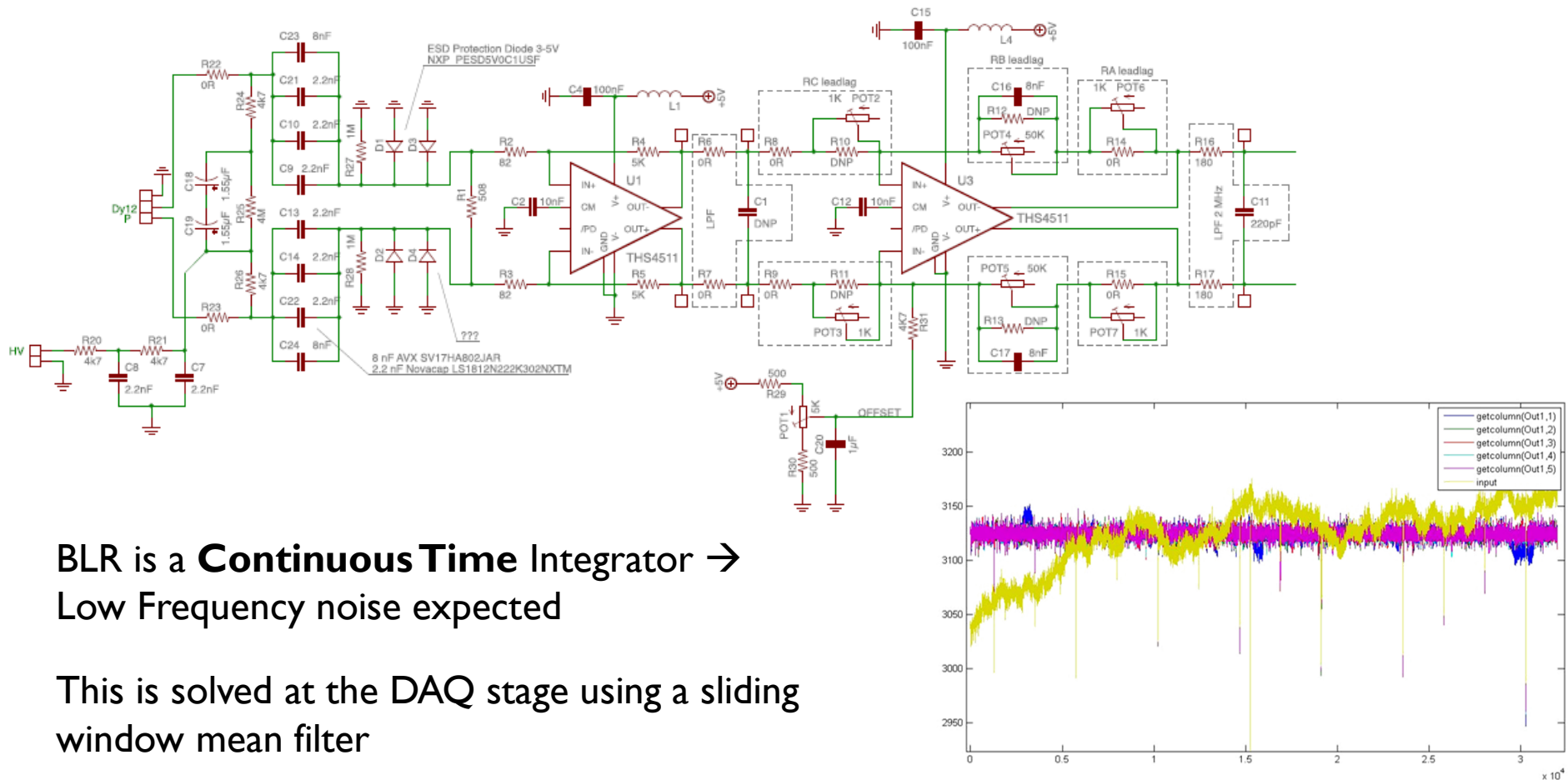- **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**




BLR is a **Continuous Time Integrator** →
Low Frequency noise expected

This is solved at the DAQ stage using a sliding window mean filter

Analog BLR Solution

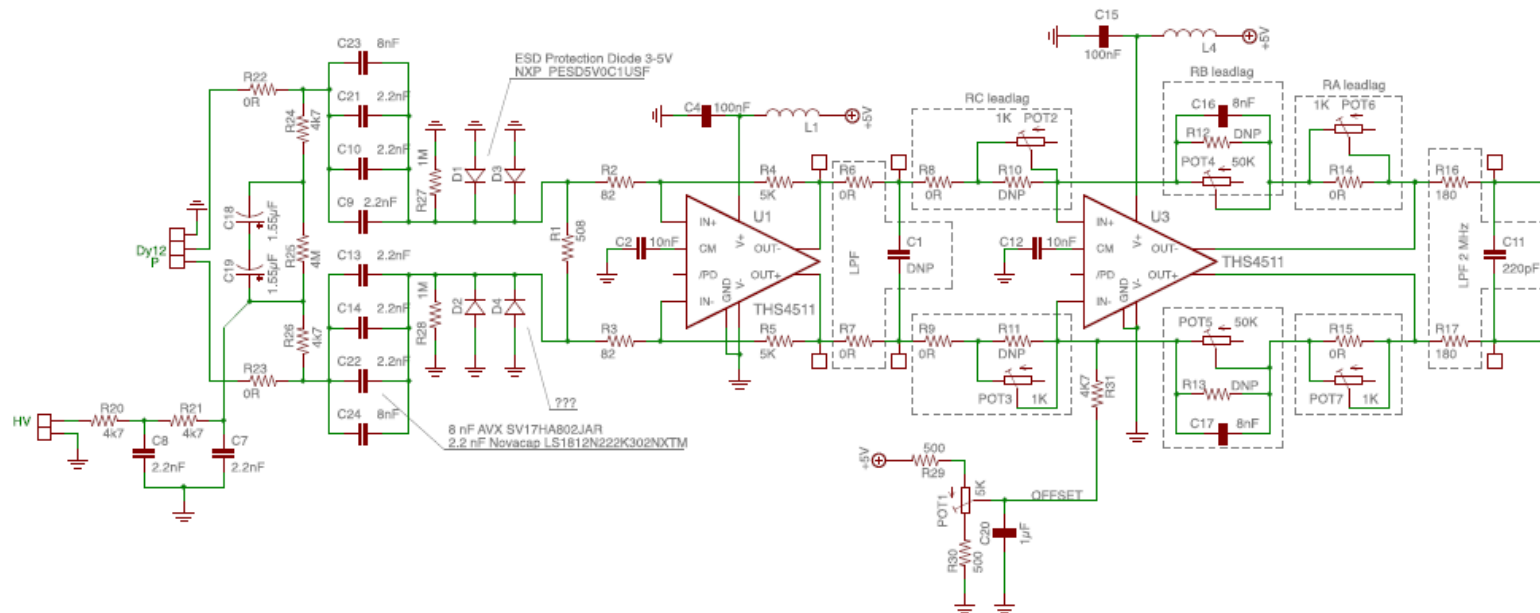- **CONCEPT: Try to fix the Coupling Capacitor effect afterwards**




BAD NEWS:



- BLR extremely difficult to trim.
- Long tails due to inaccurate pole/zero cancellation.
- BLR effect is limited to a few microseconds (no clean compensation for long pulses)

Two Sides Solution

► Moderate RC + Digital BLR

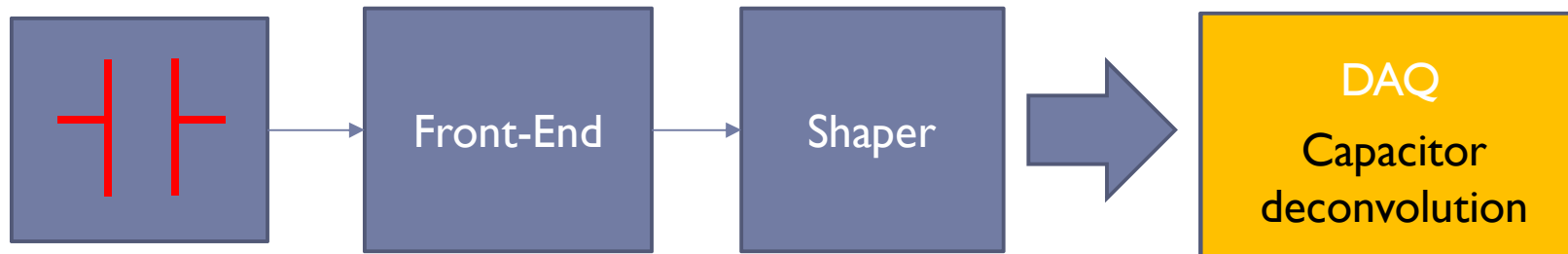

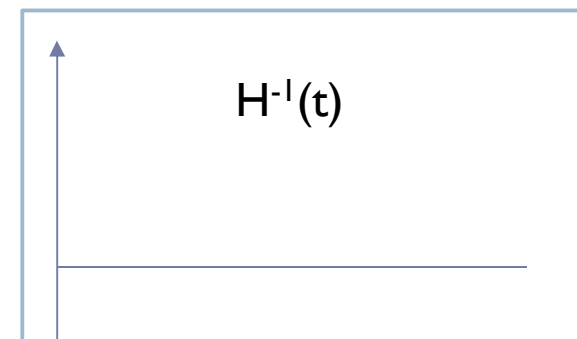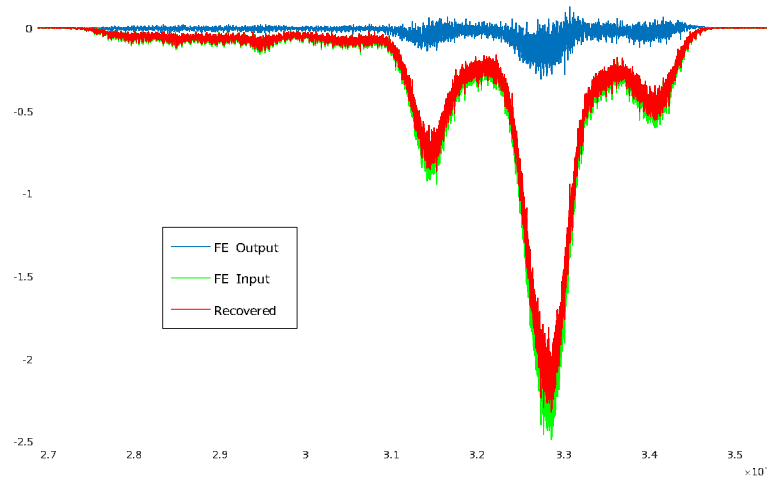FE model with Coupling C, shaping, DAQ quantization, finite precision effects and noise.




Two Sides Solution

- ▶ Moderate RC + Digital BLR

- ▶ IMPROVEMENTS:

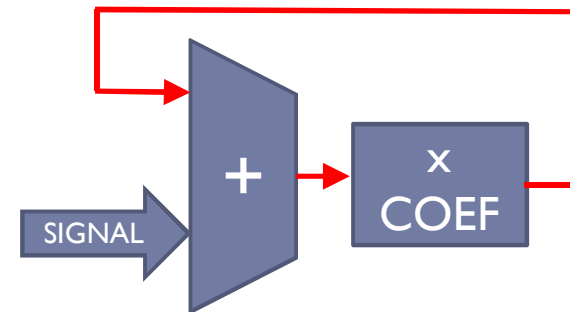- ▶ $Z_{in} \cdot C$ time constant (f_{HPB}) can be relaxed → **Lower Z_{in} → Lower NOISE**
 - ▶ Digital BLR can be switched off when no signal is detected and switched on when pulses are detected using a threshold → **No LF noise**
 - ▶ Digital BLR implementation is very simple.
NO NEED to use a FIR (MAC unit).



Two Sides Solution



► PRELIMINARY RESULTS (Simulated)

- The Zin can be downsized to 2100 Ohms with this results:

Thermal Noise* (FE OUT) < 0.17 mVrms \approx 0.43 LSB
Estimated Energy Measurement Error < 0.64 %

* Fully-Diff Opamp Config. All noise sources considered

**SPECS
FULFILLED !!!**

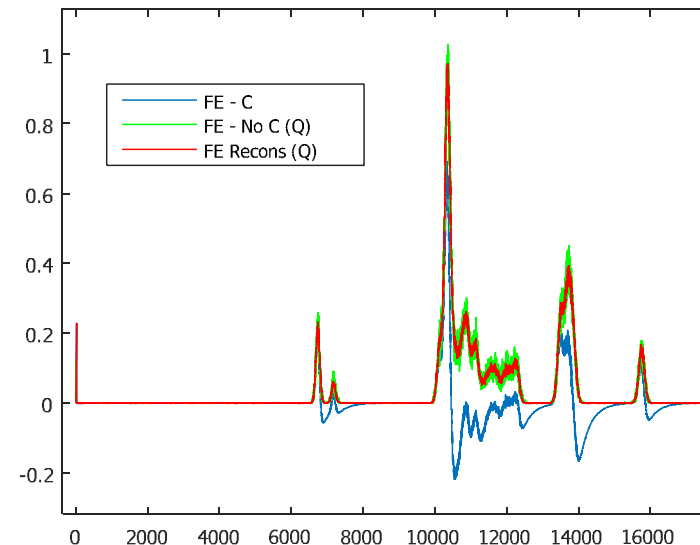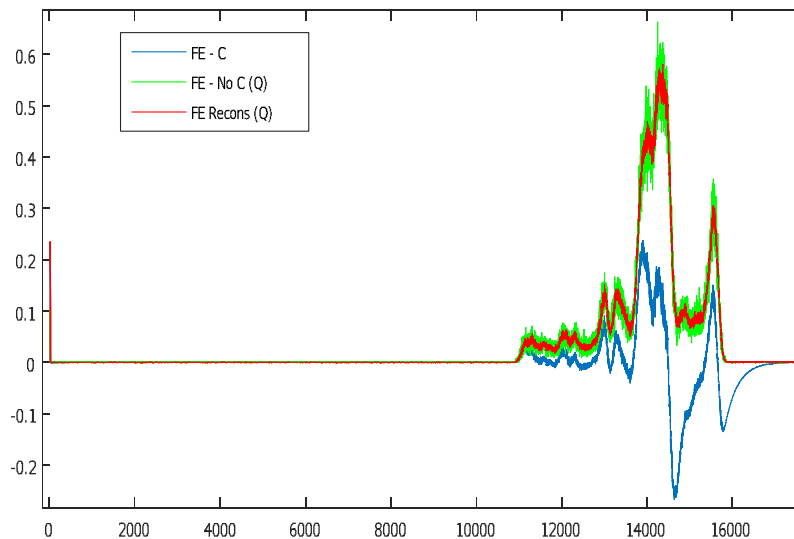

Further Improvement

► Anode Preamp + Fully Differential Mode Transmission

